

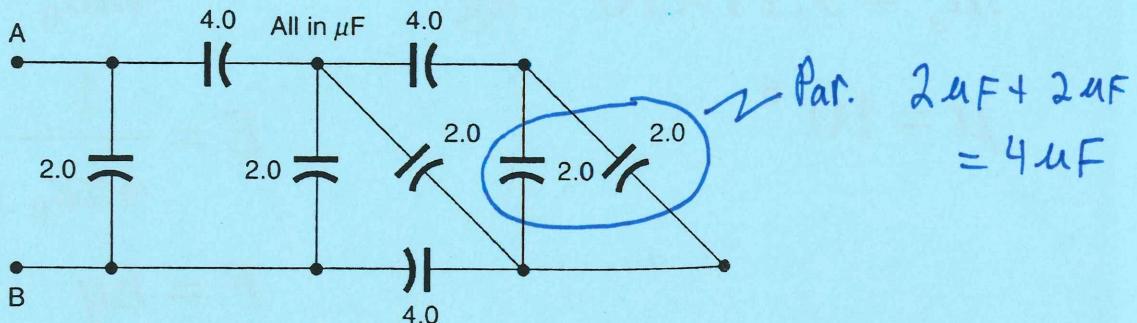
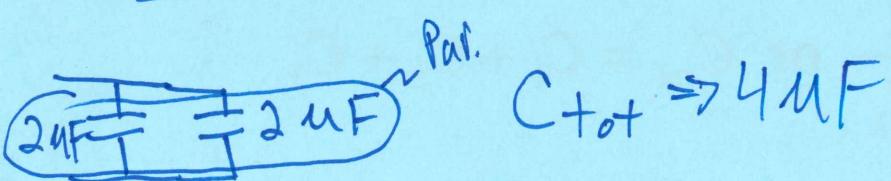
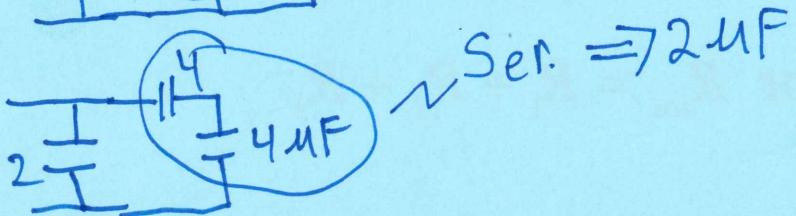
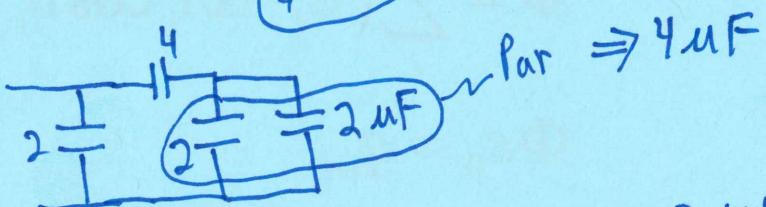
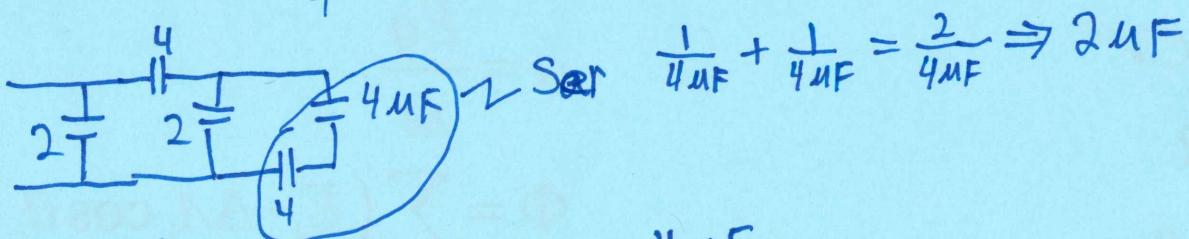


Name Charles John

Show all work in the spaces provided.

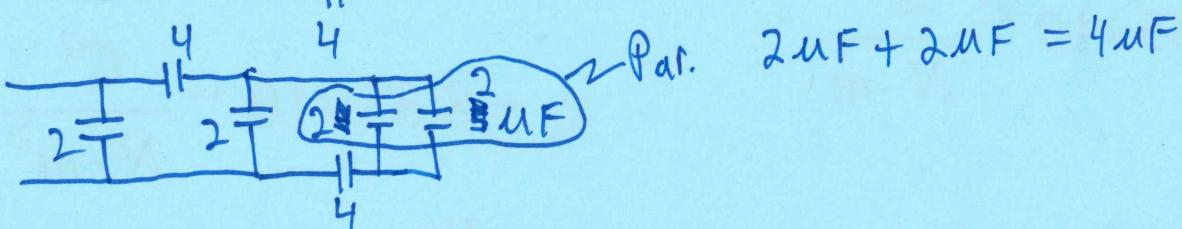


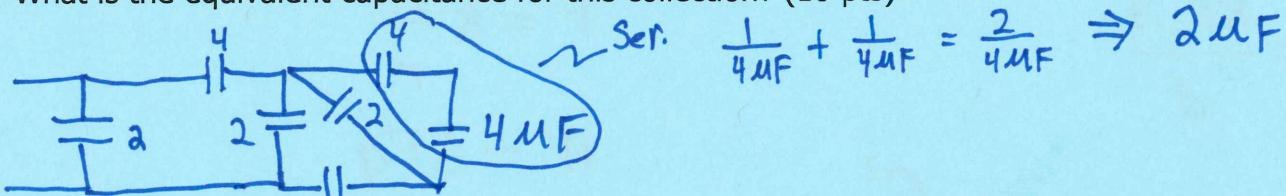- 1) What is the equivalent capacitance for this collection? (10 pts)






Name Charles Johnson

Show all work in the spaces provided.

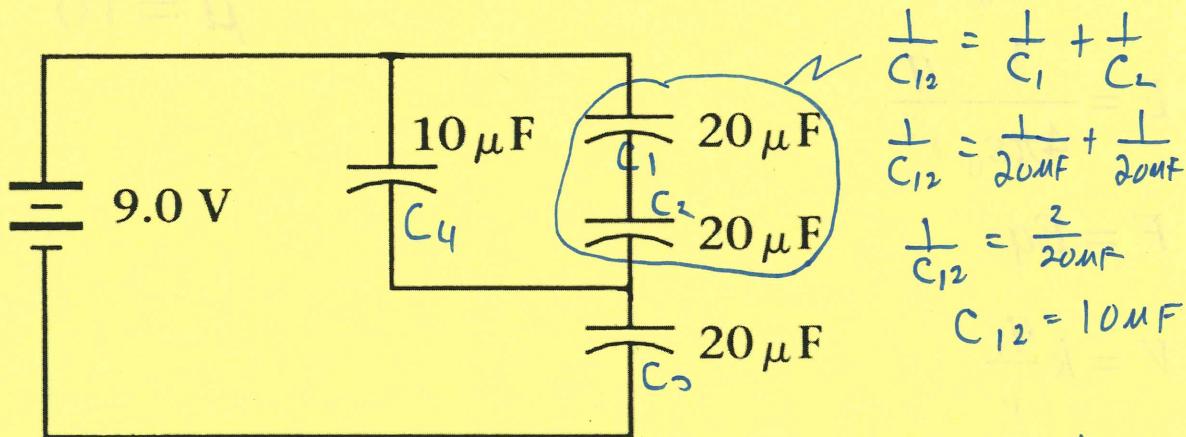

1) For the above capacitors find:

a) The equivalent capacitance. (5 pts)

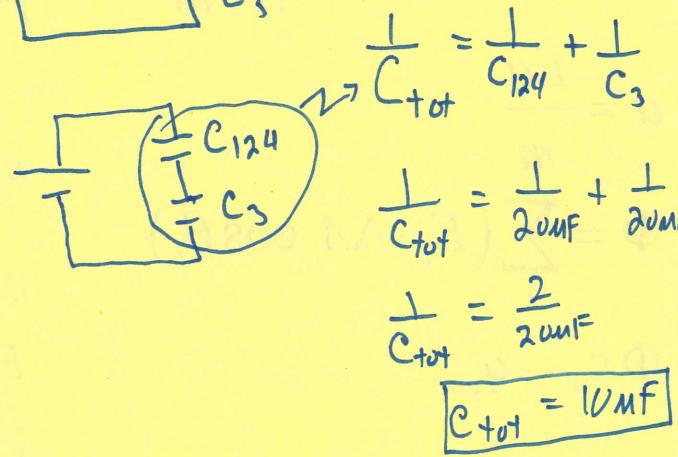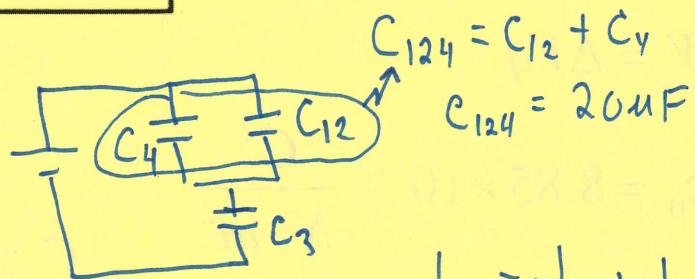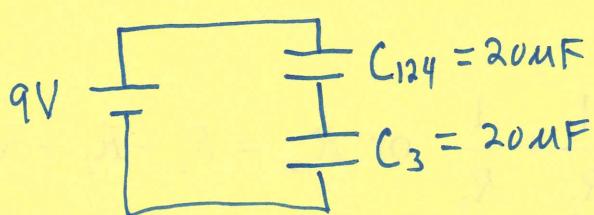b) The charge on the $10\mu F$ capacitor. (5 pts)

Series Sane q $q_3 = q_{124} = q_{tot} = C_{tot} V_{tot}$
 $= (10\mu F)(9V)$
 $= 90\mu C$

$$V_{124} = \frac{q_{124}}{C_{124}} = \frac{90\mu C}{20\mu F} = 4.5V$$

so $q_4 = C_4 V_4 = 45\mu C$ since C4 and C12 are parallel

$$V_4 = V_{124} = 4.5V$$