
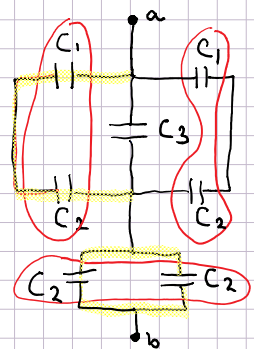


$q = CV$

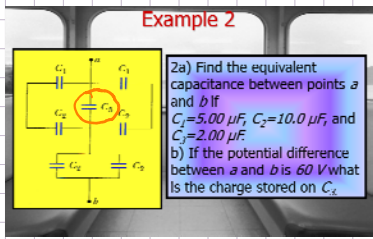

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_{12}} = \frac{1}{5\mu F} + \frac{1}{10\mu F}$$

$$\frac{1}{C_{12}} = \frac{2}{10\mu F} + \frac{1}{10\mu F}$$

$$\frac{1}{C_{12}} = \frac{3}{10\mu F}$$

$$C_{12} = \frac{10}{3} \mu F$$


$$V_3 = V_{123} = \frac{q_{123}}{C_{123}} = \frac{363 \mu C}{8.67 \mu F}$$

$$V_3 = 41.9 V$$

$$q_3 = C_3 V_3$$

$$q_3 = (2 \mu F)(41.9 V)$$

$$q_3 = 83.7 \mu C$$

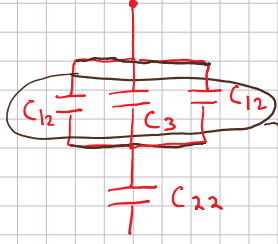

$$C_{123} = C_{12} + C_3$$

$$C_{123} = \frac{10}{3} \mu F + \frac{10}{3} \mu F + 2 \mu F$$



$$C_{123} = \frac{20}{3} \mu F + \frac{6}{3} \mu F = \frac{26}{3} \mu F$$

$$C_{123} = 8.67 \mu F$$

$$C_{22} = C_2 + C_2$$

$$C_{22} = 10 \mu F + 10 \mu F$$

$$C_{22} = 20 \mu F$$

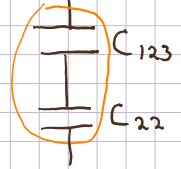
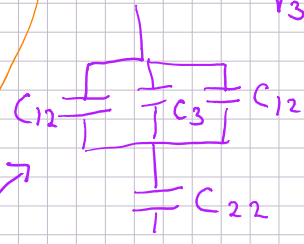


$$\frac{1}{C_{tot}} = \frac{1}{C_{123}} + \frac{1}{C_{22}}$$

$$\frac{1}{C_{tot}} = \frac{1}{8.67 \mu F} + \frac{1}{20 \mu F}$$

$$\frac{1}{C_{tot}} = .165 / \mu F$$

$$C_{tot} = 6.05 \mu F$$

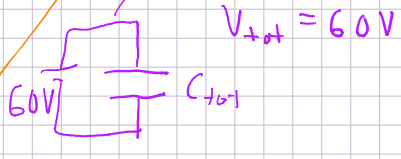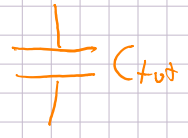

$$q_{123} = q_{22} = q_{tot}$$

$$q_{tot} = V_{tot} C_{tot}$$

$$q_{tot} = (60 V)(6.05 \mu F)$$

$$q_{tot} = 363 \mu C$$