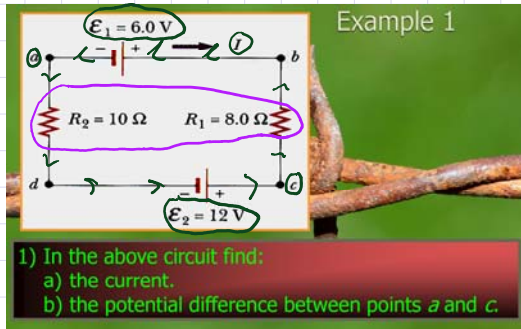



# Example 1

Sunday, March 30, 2014 4:03 PM



$$a) R_{12} = R_1 + R_2$$

$$R_{12} = 18 \Omega$$

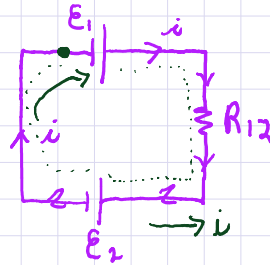

$$E_1 - i R_{12} - E_2 = 0$$

$$i R_2 = E_1 - E_2$$

$$i = \frac{E_1 - E_2}{R_2}$$

$$i = \frac{6V - 12V}{18\Omega}$$


$$i = \frac{-6V}{18\Omega} = -\frac{1}{3}A = -.333A$$

$$V_a + E_1 - i R_1 = V_c$$

$$V_c - V_a = E_1 - i R_1$$


$$\Delta V_{ca} = 6V - (-.333A)(8\Omega)$$

$$\Delta V_{ca} = 8.664V$$

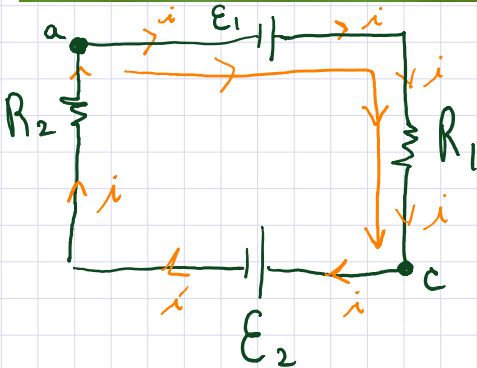


## Example 2


Monday, March 31, 2014 7:57 AM

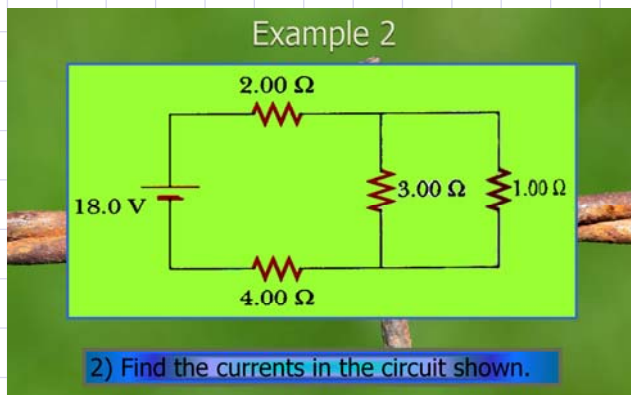
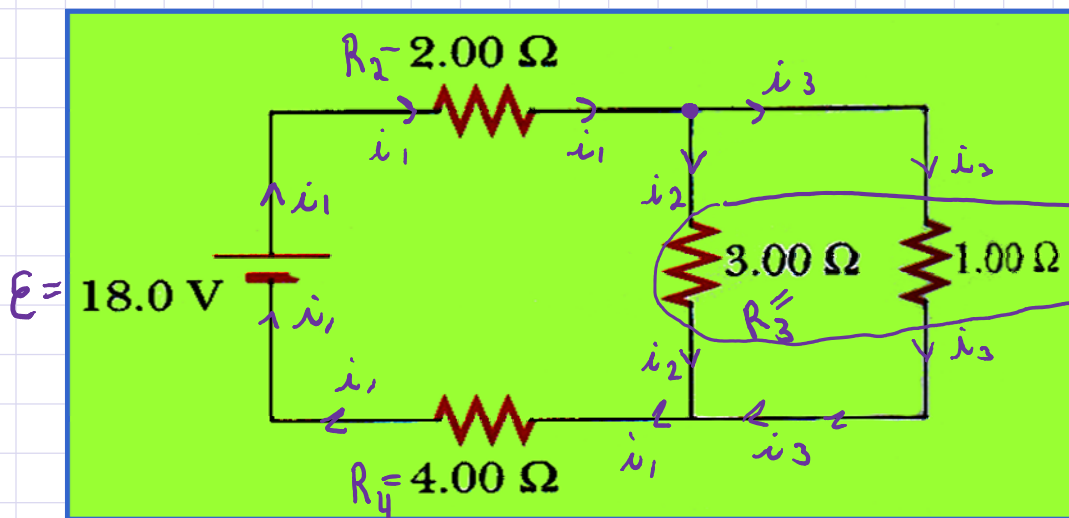
$$\begin{aligned} i_1 &= ? \\ i_2 &= ? \\ i_3 &= ? \end{aligned}$$


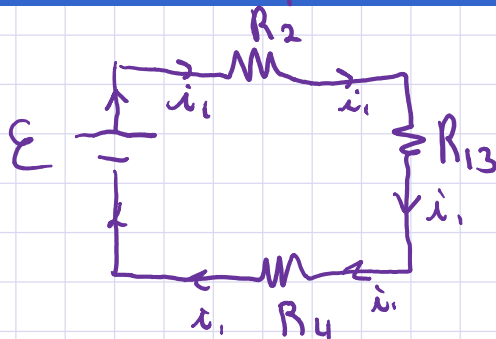
$$\begin{aligned} \frac{1}{R_{13}} &= \frac{1}{R_1} + \frac{1}{R_3} \\ \frac{1}{R_{13}} &= \frac{1}{1\Omega} + \frac{1}{3\Omega} \\ \frac{1}{R_{13}} &= \frac{3}{3\Omega} + \frac{1}{3\Omega} \\ \frac{1}{R_{13}} &= \frac{4}{3\Omega} \\ R_{13} &= \frac{3}{4}\Omega \\ &= 0.75\Omega \end{aligned}$$



$$R_{tot} = R_2 + R_4 + R_{13}$$


$$R_{tot} = 2\Omega + 4\Omega + 0.75\Omega$$


$$R_{tot} = 6.75\Omega$$



$$E = i_1 R_{tot}$$
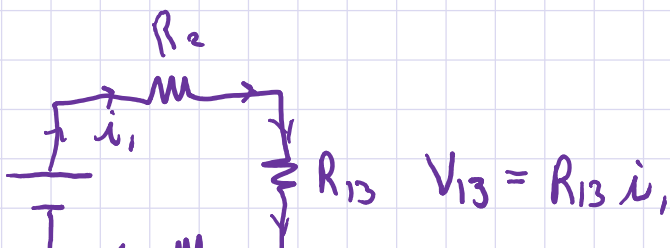
$$i_1 = \frac{E}{R_{tot}} = \frac{18V}{6.75\Omega} = 2.67A$$




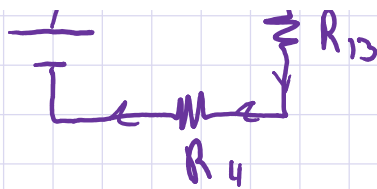

$$V_{13} = R_{13} i_1$$

$$V_{13} = (.75 \Omega)(2.67 A)$$

$$V_{13} = 2.0 V$$

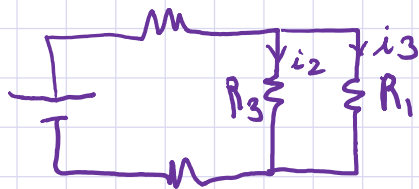

$$i = \frac{V}{R}$$

$$i_3 = \frac{V_1}{R_1} = \frac{2V}{1\Omega} = 2A$$

$$i_2 = \frac{R_2}{V_3} = \frac{2V}{3\Omega} = .67A$$

Stuff that may help!

$$F = k \frac{q_1 q_2}{r^2}$$

$$E = k \frac{q}{r^2}$$

$$V = k \frac{q}{r}$$

$$k = \frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \text{ N} \frac{\text{m}^2}{\text{C}^2}$$

$$\Delta U = \Delta V q$$

$$W = \Delta U$$

$$\Delta U + \Delta KE = 0$$

$$KE = \frac{1}{2} mv^2$$

$$F = qE$$

$$e = 1.6 \times 10^{-19} \text{ C}$$

$$m_e = 9.11 \times 10^{-31} \text{ kg}$$

$$\mu = 10^{-6}$$

$$n = 10^{-9}$$

$$C = \frac{\kappa \epsilon_0 A}{d}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}}$$

$$q = CV$$

$$E = \frac{1}{2} CV^2$$

~~$$V = iR$$~~

~~$$P = i^2 R$$~~

~~$$P = iV$$~~

$$\frac{1}{R_{tot}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \text{or} \quad R_{tot} = R_1 + R_2 + R_3$$

$$\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad \text{or} \quad C_{tot} = C_1 + C_2 + C_3$$

$$F = ma$$

# Question 1

Wednesday, March 11, 2015 7:09 AM


Review

Test 2

Review  
TEST 2

Name \_\_\_\_\_

Show all work in the spaces provided.

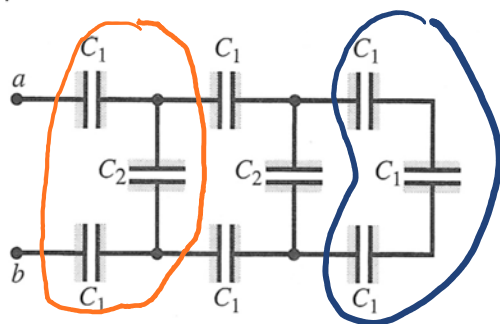


$$\frac{1}{C_{III}} = \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_1}$$

$$\frac{1}{C_{III}} = \frac{3}{C_1} = \frac{3}{6.9 \mu F}$$

$$C_{III} = \frac{6.9 \mu F}{3} = 2.3 \mu F$$

1) In the figure above each capacitance  $C_1$  is  $6.9 \mu F$  and each capacitance  $C_2$  is  $4.6 \mu F$ .

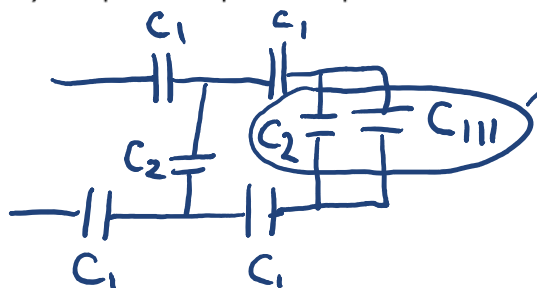
a) Compute the equivalent capacitance of the circuit between points a and b. (5 pts)



$$C_5 = C_2 + C_{III}$$

$$C_5 = 4.6 \mu F + 2.3 \mu F$$


$$C_5 = 6.9 \mu F = C_1$$

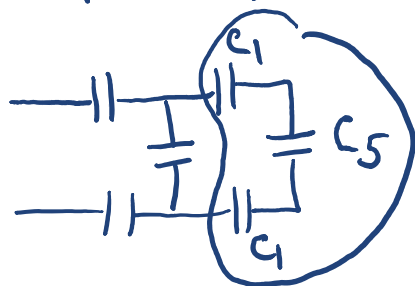

$$\frac{1}{C_6} = \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_1}$$


$$\frac{1}{C_6} = \frac{3}{C_1}$$

$$C_6 = 2.3 \mu F$$

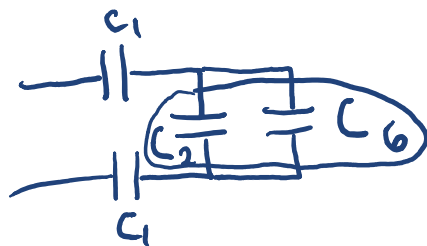


$$C_7 = C_2 + C_6$$

$$C_7 = 6.9 \mu F$$

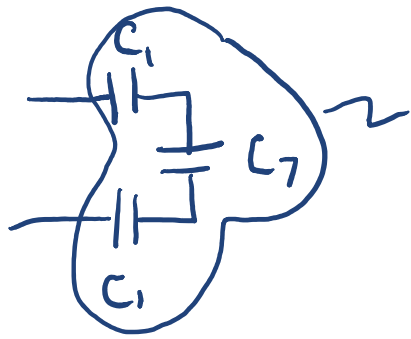

$$\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_1} + \frac{1}{C_7}$$

$$C_{tot} = 2.3 \mu F$$

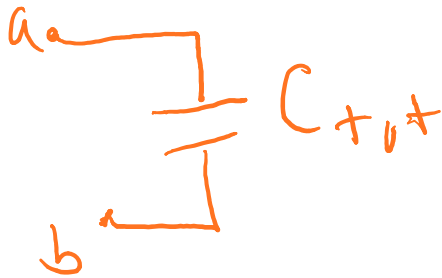

# Question 1 B

Wednesday, March 11, 2015 7:09 AM

$$q = CV$$

Review

Test 2



- b) Compute the charge on each of the three capacitors nearest a and b when the voltage between a and b is 420V. (5 pts)

$$V = 420V \quad C_{tot} = 2.3 \mu F$$

$$q_1 = q_{tot} = V C_{tot} = (420V)(2.3 \mu F)$$

$$q_1 = 966 \mu C$$

$$q = CV$$

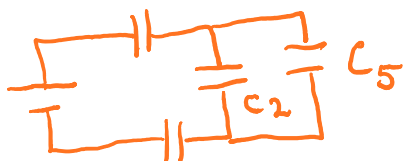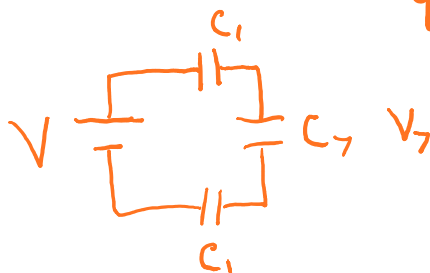

$$q_2 = C_2 V_2$$

$$V_2 = V_5 = V_7 = \frac{q_7}{C_7} = \frac{966 \mu C}{6.1 \mu F} = 140V$$

$$q_2 = (4.6 \mu F)(140V)$$

$$q_2 = 644 \mu C$$

## Question 2

Wednesday, March 11, 2015 7:09 AM

Review

Test 2

- 2) A nervous Physicist worries that two metal shelves of his wood frame bookcase might obtain a high voltage if charged by static electricity, perhaps produced by friction.

- a) What is the capacitance of the empty shelves if they have area  $0.100 \text{ m}^2$  and are  $0.200 \text{ m}$  apart? (5 pts)

$$C = \frac{\kappa \epsilon_0 A}{d} = \frac{(1) (8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}) (.1 \text{ m}^2)}{.2 \text{ m}}$$

$$C = 4.43 \times 10^{-12} \text{ F} = 4.43 \text{ pF}$$

- b) What is the voltage between them if the opposite charges of magnitude 2.00 nC are placed on them? (5 pts)

$$V = ?$$

$$q = CV$$

$$V = \frac{q}{C} = \frac{2 \times 10^{-9} \text{ C}}{4.43 \times 10^{-12} \text{ F}} = 451 \text{ V}$$






### Question 3

Wednesday, March 11, 2015 7:09 AM

Review

Test 2

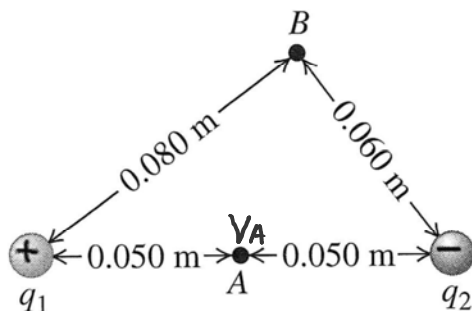

- 3) Two point charges  $q_1 = +2.4 \text{ nC}$  and  $q_2 = -6.50 \text{ nC}$  are  $0.100 \text{ m}$  apart. Point A is midway between them; point B is  $0.80 \text{ m}$  from  $q_1$  and  $0.060 \text{ m}$  from  $q_2$  (see figure above.)

a) What is the electrical potential at point A due to the charges  $q_1$  and  $q_2$ ? (3 pts)

$$V_A = k \frac{q_1}{r_1} + k \frac{q_2}{r_2} = (9 \times 10^9 \text{ N} \frac{\text{m}^2}{\text{C}^2}) \left[ \frac{2.4 \times 10^{-9} \text{ C}}{0.05 \text{ m}} - \frac{6.5 \times 10^{-9} \text{ C}}{0.05 \text{ m}} \right]$$

$$V_A = -738 \text{ V}$$

b) What is the electrical potential at point B due to the charges  $q_1$  and  $q_2$ ? (3 pts)

$$V_B = k \frac{q_1}{r_1} + k \frac{q_2}{r_2} = (9 \times 10^9 \text{ N} \frac{\text{m}^2}{\text{C}^2}) \left[ \frac{2.4 \times 10^{-9} \text{ C}}{0.08 \text{ m}} - \frac{6.5 \times 10^{-9} \text{ C}}{0.06 \text{ m}} \right]$$

$$V_B = -705 \text{ V}$$

c) What is the work done by the electric field on a charge of  $2.50 \text{ nC}$  that travels from point B to Point A? (4 pts.)

$$W = \Delta V q = (V_f - V_i) q = (V_A - V_B) q = [-738 \text{ V} - (-705 \text{ V})] (2.5 \times 10^{-9} \text{ C})$$

$$W = 8.25 \times 10^{-8} \text{ J}$$

## Question 4


Wednesday, March 11, 2015 7:11 AM

Review

Test 2

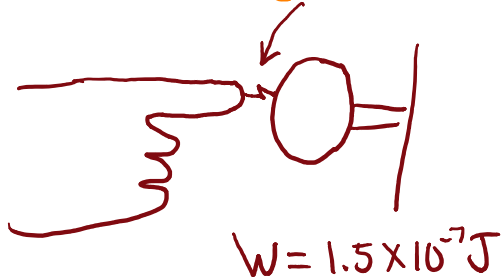- 4) Just as you touch a metal door knob, a spark of electricity (electrons) jumps from your hand to the knob. The electrical potential of the knob is greater than that of your hand. The work done by the electric force on the electrons is  $1.5 \times 10^{-7} \text{ J}$ . How many electrons jump from your hand to the knob? (10 pts)

$$\Delta V = 3 \times 10^4 \text{ V (given)}$$



$$W = \Delta V q$$

$$q = \frac{W}{\Delta V} = \frac{1.5 \times 10^{-7} \text{ J}}{-3 \times 10^4 \text{ V}}$$

$$q = -5 \times 10^{-12} \text{ C}$$

$$\# \text{ el} = \frac{-5 \times 10^{-12} \text{ C}}{-1.6 \times 10^{-19} \text{ C}}$$

$$q_e = -1.6 \times 10^{-19} \text{ C}$$

$$\frac{q}{q_e} = \# \text{ el}$$

$$= \boxed{3.13 \times 10^7}$$